


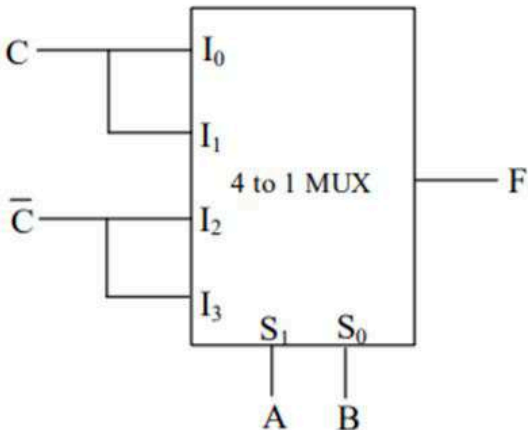
Dr. B.R.Ambedkar Institute of Technology
Recruitment for the Post of Lab Technician (ECE)

Date of Examination: 17/05/2025

Exam Time: 10:00 AM - 11:00 AM

Exam Slot: A1


#	Question ID	Question	Answer Key
1	5292	The output of a diode detector contains a. D.C. voltage b. modulating signal c. RF ripple d. all of the above	
2	5285	The image channel selectivity of super heterodyne receiver depends upon a. IF amplifiers only b. RF and IF amplifiers only c. Pre selector, RF and IF amplifiers d. Pre selector and RF amplifiers	
3	5298	The nature of calibration signal in a CRO is (1) sawtooth (2) square (3) sinusoidal (4) Triangular	
4	5343	A diode for which you can change the reverse bias, and thus vary the capacitance is called a a. varactor diode b. tunnel diode c. zener diode d. switching diode	
5	5283	In FM broadcasting, the peak frequency deviation and the maximum audio frequency handled, are respectively a. 75 kHz ; 10 kHz b. 75 kHz ; 15 kHz c. 200 kHz ; 10 kHz d. 75 kHz ; 5 kHz	
6	5337	ASK, FSK and PSK are examples of _____ encoding a. Digital to Digital b. Digital to Analog c. Analog to Analog d. Analog to Digital	


7	5264	<p>The following GATE is equivalent to</p>  <p>a. OR gate b. AND gate c. NOR gate d. EXOR gate</p>	
8	5300	<p>The smallest change in measured value to which the instrument will respond is known as</p> <p>a. Accuracy b. Precision c. Resolution d. Sensitivity</p>	
9	5257	<p>The logic realized by the circuit shown in figure is:</p>  <p>a. $F = A \odot C$ b. $F = A \oplus C$ c. $F = B \odot C$ d. $F = B \oplus C$</p>	
10	5279	<p>In a class B amplifier, it is found that D.C. power is 25 W, find the A.C. power.</p> <p>a. 10 W b. 62.5 W c. 25 W d. 50 W</p>	
11	5271	<p>In a multi-stage RC coupled amplifier the coupling capacitor</p> <p>a. limits the high frequency response b. limits the low frequency response c. blocks the d.c. components d. limits the frequency components</p>	
12	5290	<p>When the modulation index is halved, it is found that the antenna current (r.m.s. value) is also halved. The type of modulation used is</p> <p>a. AM (carrier plus both sidebands) b. Single sideband plus carrier c. SSB-SC d. Vestigial sideband</p>	


13	5261	<p>The Q' (complement of Q) of last FF of 4 stage shift register is connected to input of the first FF, then the logic circuit acts as</p> <ol style="list-style-type: none"> Modulo 4 counter Modulo 10 counter Modulo 16 counter Modulo 8 counter 	
14	5250	<p>Transformer utilisation factor of a half wave rectifier is ____</p> <ol style="list-style-type: none"> 0.234 0.279 0.287 0.453 	
15	5338	<p>The most important disadvantage of CDMA over TDMA is that</p> <ol style="list-style-type: none"> There should be no precise time co-ordination among various simultaneous transmitters Message delay is lower CDMA needs lower bandwidth than TDMA Hardware requirement is lower than in TDMA 	
16	5274	<p>Crystal oscillator is used because</p> <ol style="list-style-type: none"> it gives high output voltage the frequency of oscillation is constant it works well at high frequency It requires low d.c. supply voltage 	
17	5321	<p>Slew rate is defined as</p> <ol style="list-style-type: none"> Rate of change of output voltage per unit time Maximum voltage output Minimum input signal Bandwidth of the amplifier 	
18	5265	<p>What is the simplified expression for $z = AB'C' + AB'C + ABC$ is</p> <ol style="list-style-type: none"> $A(B' + C)$ $A'(B + C)$ AC' $A(B + C)$ 	
19	5248	<p>The relation between α and β is</p> <ol style="list-style-type: none"> $\beta = \alpha / (1 - \alpha)$ $\alpha = \beta / (1 + \beta)$ $\beta = \alpha / (1 + \alpha)$ $\alpha = \beta / (1 - \beta)$ 	
20	5278	<p>The maximum theoretical efficiency of a Class A amplifier can be</p> <ol style="list-style-type: none"> 50% 78% 25% None of above 	

21	5318	<p>In an op-amp integrator circuit, the output voltage is proportional to the_____</p> <ol style="list-style-type: none"> cube of the input signal sum of the input signal integral of the input signal derivative of the input signal 	
22	5270	<p>Darlington pair consists of the following two stages</p> <ol style="list-style-type: none"> both CE CE and CB CE and CC both CC 	
23	5324	<p>What is the function of the 555 Timer in monostable mode?</p> <ol style="list-style-type: none"> Generates a continuous square wave Generates a single pulse when triggered Works as an amplifier Works as a voltage regulator 	
24	5340	<p>A comparison of FDM and TDM system show that</p> <ol style="list-style-type: none"> FDM requires a lower bandwidth but TDM has great Noise immunity FDM has great noise immunity and requires lower BW than TDM FDM requires channel synchronization, While TDM has greater noise immunity FDM requires more multiplexing while TDM requires band pass filter 	
25	5334	<p>Which one is more efficient in terms of BW</p> <ol style="list-style-type: none"> QAM FSK BPSK M-ARY PSK 	
26	5246	<p>For a fixed bias circuit having $R_C=4.7K\Omega$ and $R_B=1K\Omega$, $V_{CC}=10V$, and base current at Bias point was found to be $0.2\mu A$, Find β?</p> <ol style="list-style-type: none"> 100 106 125 0 	
27	5301	<p>Voltmeter has a loading effect in a particular circuit. This leads to</p> <ol style="list-style-type: none"> Static error Dynamic error Gross error Random error 	
28	5320	<p>For an ideal OP-AMP, which of the following is correct?</p> <ol style="list-style-type: none"> Zero input impedance and infinite output impedance Infinite input impedance and infinite output impedance Infinite input impedance and zero output impedance Zero input impedance and zero output impedance 	

29	5245	<p>Which of the following equation represents mass action law for semiconductors in electronic circuits</p> <ol style="list-style-type: none"> $n \times p = n_i^2$ $n \times p = n_i$ $n \times p = n_i^3$ $n \times p = n_i^{1/2}$ 	
30	5327	<p>Which of the following pulse modulation system is Analog</p> <ol style="list-style-type: none"> PCM Differential PCM PWM Delta 	
31	5249	<p>To use FET as a voltage-controlled resistor, in which region it should operate?</p> <ol style="list-style-type: none"> Ohmic region cut off Saturation cut off and saturation 	
32	5281	<p>The working of SMPS is based on:</p> <ol style="list-style-type: none"> Integral control principle Frequency control principle Chopper principle Phase control principle 	
33	5263	<p>Minimum of NAND Gates required to implement the following Boolean function is</p> $F(x, y, z) = \sum m(2, 3, 4, 5)$ <ol style="list-style-type: none"> 5 4 6 7 	
34	5331	<p>The frequency is shifted between two levels in which of following</p> <ol style="list-style-type: none"> ASK FSK PSK QAM 	
35	5275	<p>The change in output voltage for the corresponding change in load current in a 7805 IC regulator is defined as</p> <ol style="list-style-type: none"> All of the mentioned Line regulation Load regulation Input regulation 	
36	5325	<p>In the circuit of an Op-Amp as an integrator, the feedback circuit mainly contains a</p> <ol style="list-style-type: none"> Resistor Capacitor Diode Transistor 	

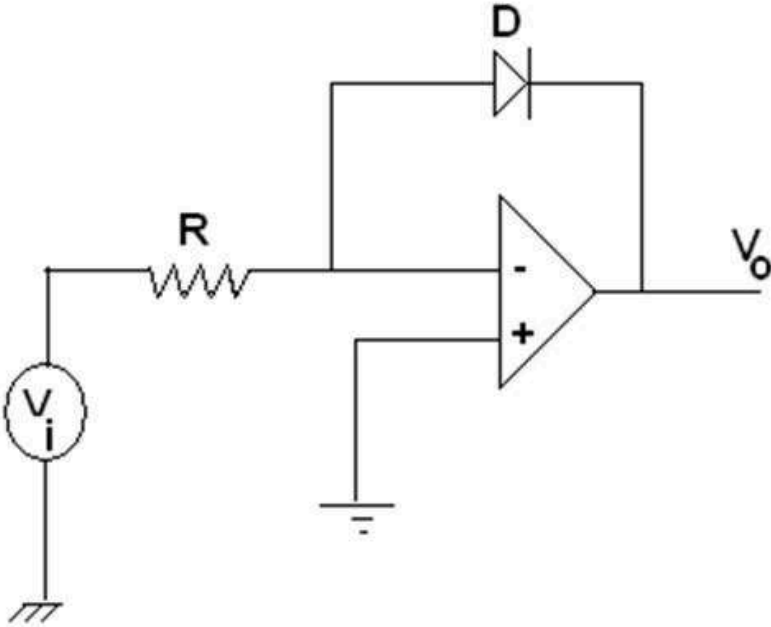37	5287	<p>Which of the following schemes suffer(s) from the threshold effect?</p> <ol style="list-style-type: none"> AM detection using envelope detection AM detection using synchronous detection FM detection using discriminator SSB detection using synchronous detection 	
38	5317	<p>The circuit shown in the figure can be used as a</p>  <ol style="list-style-type: none"> full wave rectifier voltage to frequency converter logarithmic amplifier frequency to voltage converter 	
39	5272	<p>The gain of a transistor amplifier falls at high frequency due to the</p> <ol style="list-style-type: none"> coupling capacitor at the output skin effect internal capacitances of device coupling capacitor at the input 	
40	5268	<p>One of the conditions of oscillation is</p> <ol style="list-style-type: none"> Phase shift is 90 degrees Phase shift is 180 degrees Phase shift is 0 degrees Phase shift is 45 degrees 	
41	5276	<p>Which of the following component gives smooth DC output?</p> <ol style="list-style-type: none"> Clamper Regulator Clipper Rectifier 	

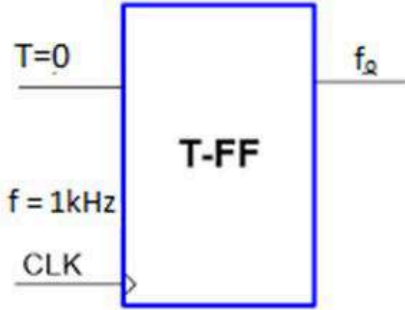42	5302	<p>which of the following instrument is based on 'See back effect'</p> <ol style="list-style-type: none"> PMMC Potentiometer Electro dynamometer Thermo couple instrument 	
43	5252	<p>In the saturated region, the transistor acts like a _____</p> <ol style="list-style-type: none"> poor transistor amplifier open switch closed switch 	
44	5253	<p>The number of full and half-adders required to add 32-bit numbers is</p> <ol style="list-style-type: none"> 16 half-adders, 16 full-adders 1 half-adder, 31 full-adders 32 half-adders, 0 full-adders 8 half-adders, 24 full-adders 	
45	5255	<p>58. The input frequency for the FF given is 1 KHz, then what will be output frequency</p>  <ol style="list-style-type: none"> 50 Hz 1 kHz 0 Hz 2 KHz 	
46	5266	<p>Which of the following counter is also called as asynchronous counter?</p> <ol style="list-style-type: none"> Decimal counter Ripple counter BCD counter LSI counter 	
47	5335	<p>To demodulate PAM, the following circuit is used</p> <ol style="list-style-type: none"> High pass filter Low pass filter LC circuit OP-Amp 	
48	5339	<p>In a communication system, noise is most likely to affect the signal</p> <ol style="list-style-type: none"> In the transmitter In the channel In the formation source At the destination 	

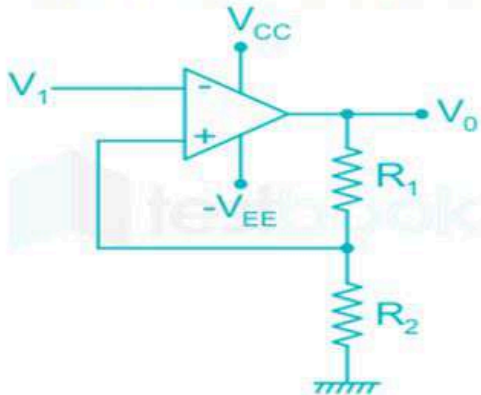49	5288	<p>Flat top sampling of low pass signals</p> <ol style="list-style-type: none"> Gives rise to aperture effect Implies oversampling Leads to aliasing Introducing delay distortion 	
50	5311	<p>A thermocouple is A_____ type transducer</p> <ol style="list-style-type: none"> variable resistance variable generating variable inductance variable divider 	
51	5315	<p>The maximum rate of change of the output voltage in response to step input voltage is known as _____ of an op-amp.</p> <ol style="list-style-type: none"> CMRR Offset voltage Slew rate Voltage gain 	
52	5310	<p>The LVDT usually has two secondaries connected in</p> <ol style="list-style-type: none"> series addition series opposition parallel opposition parallel addition 	
53	5342	<p>In Zener Diode, Increasing Doping Level leads</p> <ol style="list-style-type: none"> to increase the Zener Potential to decrease the Zener Potential Zener Potential remains constant Zener Potential Independent of doping 	
54	5319	<p>What does the following diagram represent?</p>  <ol style="list-style-type: none"> Bistablemultivibrator Astable vibrator Monostable vibrator Schmitt trigger 	

55	5294	<p>Which of the following is same in AM and FM receivers</p> <ol style="list-style-type: none"> Demodulator AGC IF amplifier All of the above 	
56	5280	<p>The cross-over distortion behaviour characteristic of:</p> <ol style="list-style-type: none"> class-A output stage common base output stage class AB output stage class B output stage 	
57	5314	<p>A stable multivibrator has</p> <ol style="list-style-type: none"> A stable multivibrator has one stable state two stable state two quasi-stable states 	
58	5312	<p>An ideal Op-Amp slew rate is</p> <ol style="list-style-type: none"> very slow slow fast infinitely fast 	
59	5308	<p>A linear variable differential transformer (LVDT) has____</p> <ol style="list-style-type: none"> Two primary windings Movable magnetic core 3 secondary windings zero output voltage 	
60	5242	<p>FET is a</p> <ol style="list-style-type: none"> Current controlled device Voltage controlled device Both current and voltage controlled device Normal device 	

Dr B.R Ambedkar Institute of Technology
Answer Key

Post: Lab Technician (Electronics & Communication Engineering)

Date of Exam: 17.5.25 Exam Time :2:00PM – 3.00PM Exam Slot :A2

Post: Lab Technician (Electronics & Communication Engineering)

Question No	ID No.	Option
1	5292	D
2	5285	B
3	5298	B
4	5343	A
5	5283	B
6	5337	A
7	5264	A
8	5300	C
9	5257	A
10	5279	C
11	5271	B
12	5290	C
13	5261	B
14	5250	C
15	5338	A
16	5274	B
17	5321	A
18	5265	A
19	5248	B
20	5278	A
21	5318	C
22	5270	D
23	5324	B
24	5340	C
25	5334	A
26	5246	B
27	5301	C
28	5320	C
29	5245	A
30	5327	C
31	5249	A
32	5281	C
33	5263	D
34	5331	B
35	5275	C
36	5325	B
37	5287	C
38	5317	C
39	5272	C
40	5268	A
41	5276	B
42	5302	D

43	5252	D
44	5253	A
45	5255	C
46	5266	B
47	5335	B
48	5339	B
49	5288	A
50	5311	C
51	5315	D
52	5310	B
53	5342	B
54	5319	D
55	5294	C
56	5280	D
57	5314	C
58	5312	D
59	5308	B
60	5242	D